



17 APRIL 2022

# PROJECT REPORT

CMPN301 Phase 1

## PRESENTED BY

Youssef Mahmoud Zakaria 1180029

Karim Ahmed Shawky 1180484

Mahmoud Mohamed Ezz ElDin 1180134

Khaled Mahmoud Mohamed 1180105

# Table of Contents

03 Instruction Format


04 Instruction Format (Cont.)

05 Schematics

09 Pipeline Stages
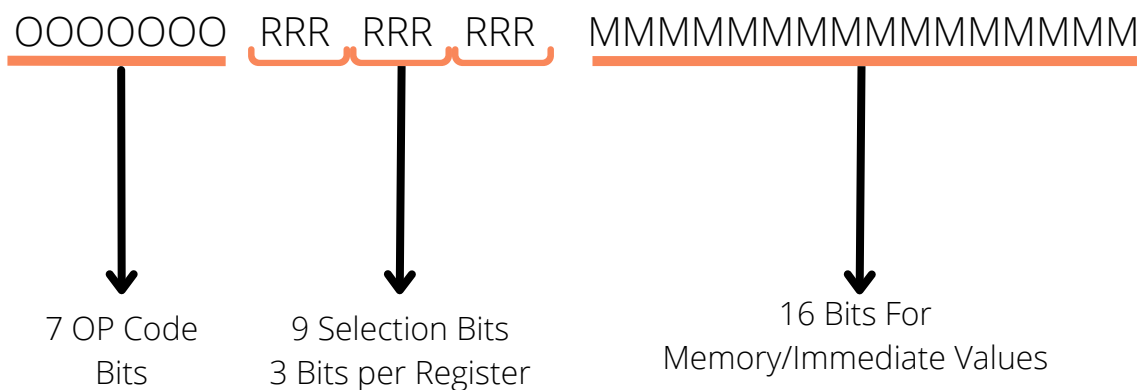
# Instruction Format

Each Instruction is 32 bits, where the Last 16 bits are mainly used for memory addresses or Immediate values. 9 bits in the middle are used mainly for register selection and the first 7 bits are used to decode instructions.




NO PROBLEMS OP CODE	00000XX	Rdst	Rsrc1	Rsrc2	Imm/Address
NOP	0000000	-	-	-	-
HLT	0000001	-	-	-	-
SETC	0000010	-	-	-	-
FULL FORWARDING OP CODES	01XXXXX				
NOT	0100000	RRR	-	-	-
INC	0100001	RRR	-	-	-
POP	0100010	RRR	-	-	-
IN	0100011	RRR	-	-	-
MOV	0100100	RRR	RRR	-	-
SWAP	0100101	RRR	RRR	-	-
ADD	0100110	RRR	RRR	RRR	-
SUB	0100111	RRR	RRR	RRR	-
AND	0101000	RRR	RRR	RRR	-
IADD	0101001	RRR	RRR	-	16bits

MEMORY (LOAD USE CASE)	1xxxxxx				
LDM	1000000	RRR	-	-	16bits
LDD	1000001	RRR	RRR	-	16bits
STD	1100000	-	RRR	RRR	16bits
OUT	1100001	-	-	-	-
PUSH	1100010	-	-	-	-
JZ	1100011	-	-	-	16bits
JN	1100100	-	-	-	16bits
JC	1100101	-	-	-	16bits
JMP	1100110	-	-	-	16bits
CALL	1100111	-	-	-	16bits
RET	1101000	-	-	-	-
INT	1101001	-	-	-	-
RTI	1101010	-	-	-	-


# Schematics

## BLOCKS, AND DATA-FLOW CONNECTIONS


### Fetching Instructions

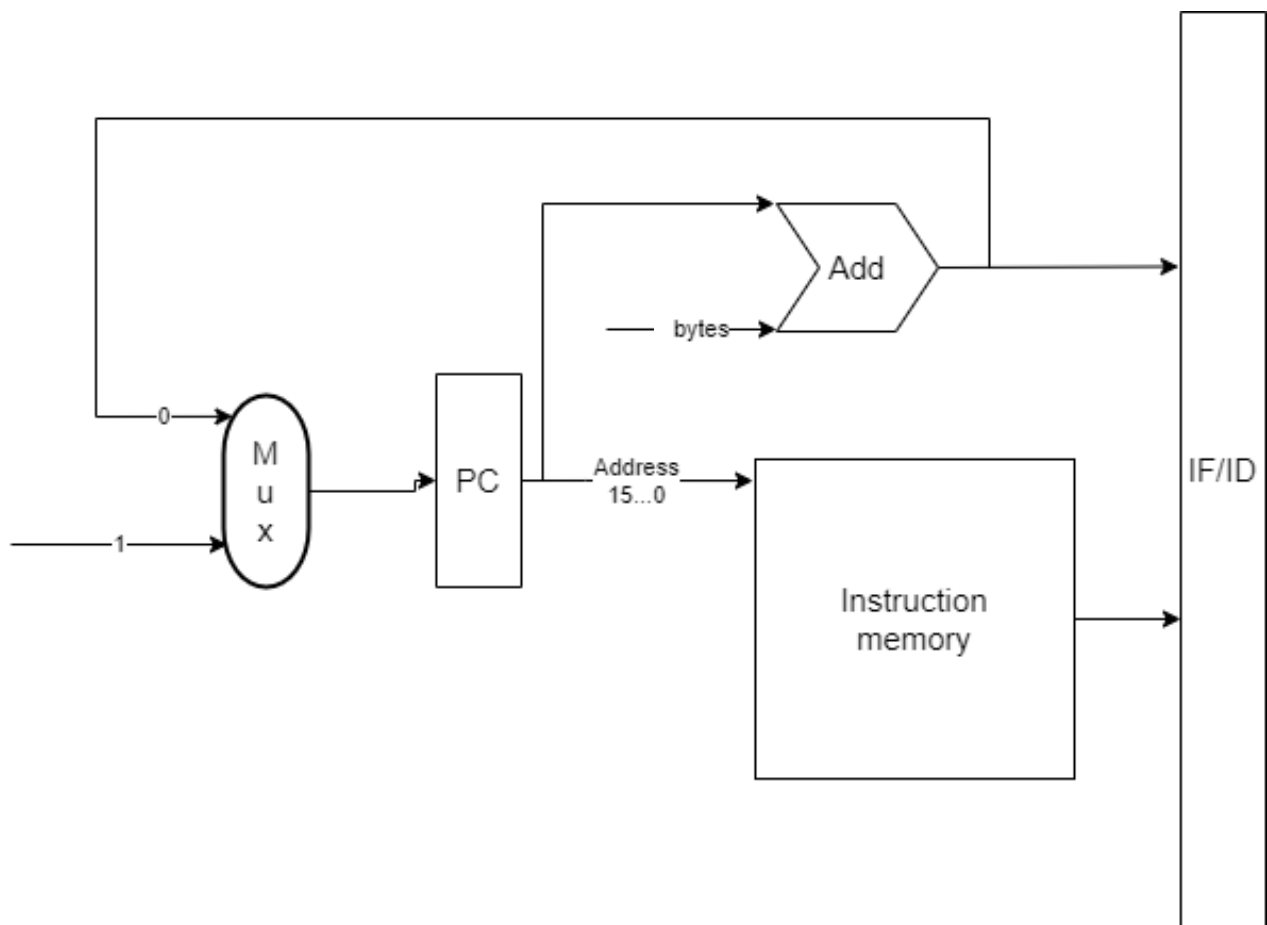

# MEMORY

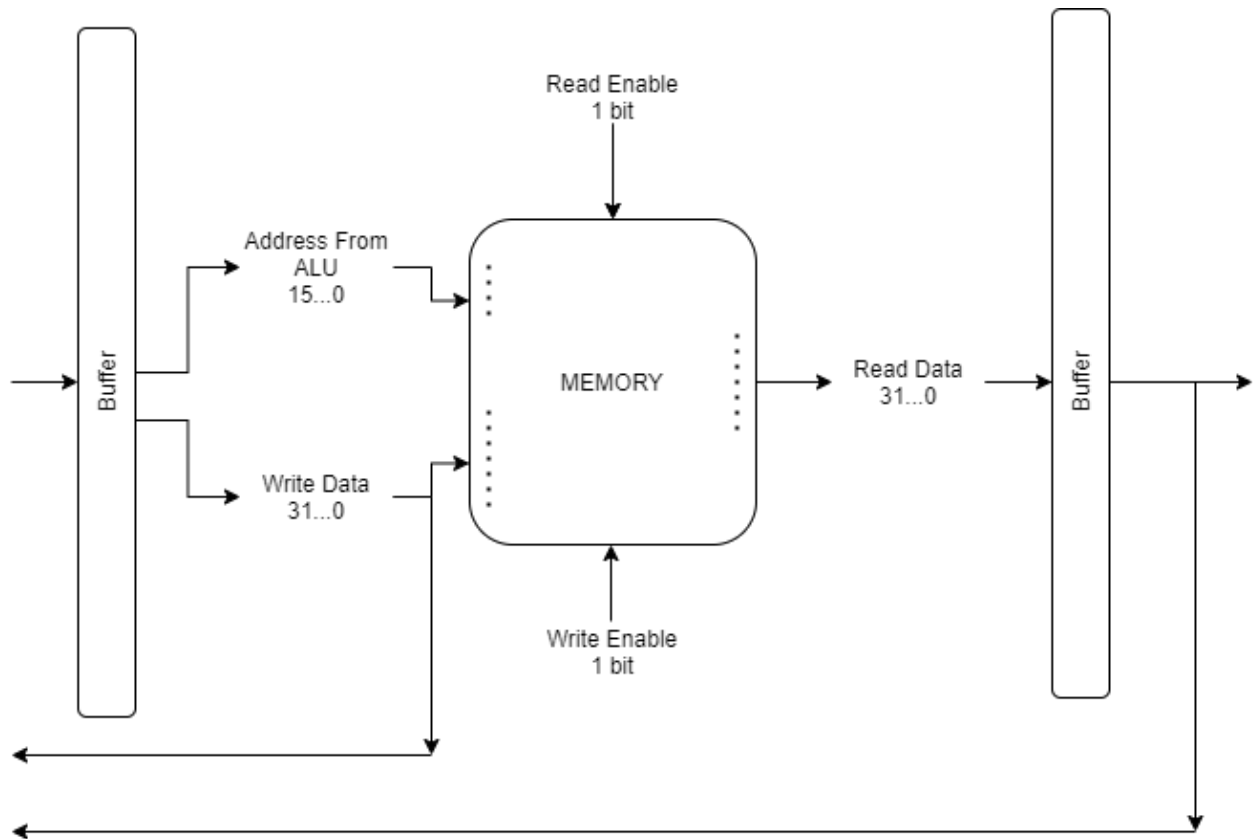

# ALU

 

# Control Unit

## Examples of Control signals:

- Alu Enable
- Alu Operations
- Memory Read and write Enables
- Forwarding unit
- Write Back Selector
- Write Back Rdist decoder
- Register selector
- Buffers enable
- Buffers Hlt/reset
- branching mux
- in and out ports enables
- stack enables


### Control unit function:

The control unit checks the provided opcode when a certain opcode is found, corresponding enables are set, and so on. The Control unit also keeps track of the forwarding process and manages some of the hazards if detected.

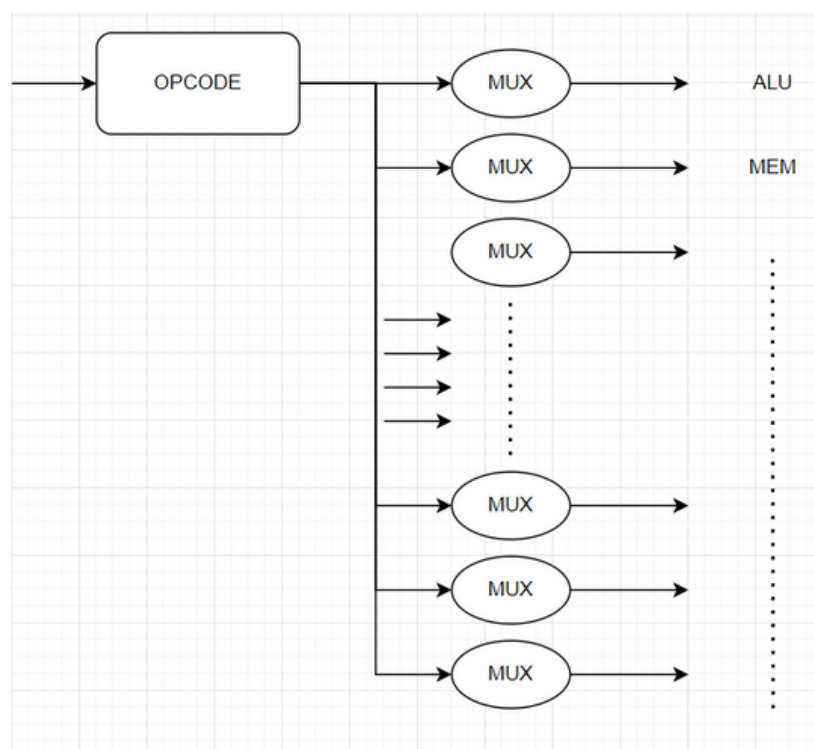
### Example:

AND Operation when detected, the control unit sends the anding operation to the ALU and sets enable to 1, this means that the Alu will AND its 2 operands.

Control Unit is a collection of multiplexers that depend on the OPCODE:



# Full Connected Schematic

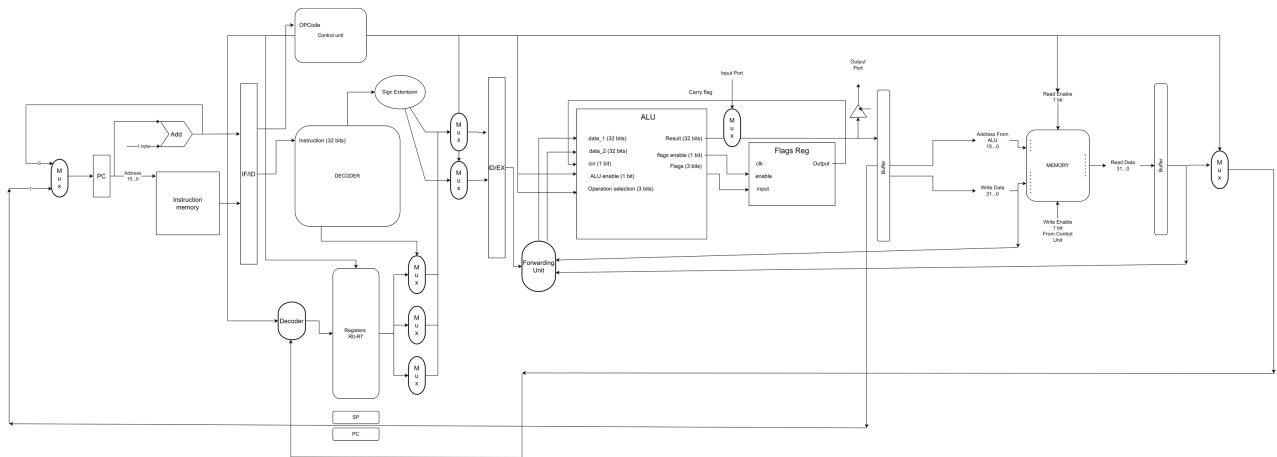



# Pipeline Stages

## REGISTER DETAILS AND HAZARDS

Pipeline hazard solutions:

- Full Data forwarding (alu and mem) is used alongside a forwarding unit.
- Static branch prediction is used (assuming Not Taken)
  - load new instructions until alu determine if the branch is taken or not
  - if not taken, continue
  - if taken, flush the pipe and jump to new instruction

Pipeline register details:

- IF/ID:
  - 32-bit instruction
  - 32-bit PC
- ID/EX:
  - 3-bit Rdst decoder
  - 32-bit Rsrc1
  - 32-bit Rsrc2
  - Control Signals
- EX/MEM
  - 32-bits Result
  - Control Signals
  - 32-bit Rsrc1
- MEM/WB
  - Control Signals (contains Rdst)
  - 32-bit ALU Result
  - 32-bit Mem Read